

DP Computer Science: A 1.2.5 Logic Diagrams

1. Core Concepts & Learning Objectives

Learning Intentions

By the end of this lesson, students will be able to:

- **Construct** a logic diagram from a Boolean expression, using the correct standard symbol for each of the seven gates and labelling every input and the output
- **Trace** a set of inputs through a logic diagram to produce its output
- **Construct** the diagram for a combination of gates that performs a more complex operation, such as the **half adder**
- **Simplify** a logic diagram or expression by applying the laws of Boolean algebra, naming the law used at each step

Command Term Note: The lesson is held at **Construct**—students actually draw circuits and simplify expressions. XNOR is now included (full set of seven gates). Boolean algebra laws and diagram construction are taught here, not in A1.2.4.

Key Vocabulary (Tier 3)

Term	Definition
Logic diagram	A drawing of a circuit as gates joined by wires, with signals flowing left to right
Standard gate symbol	The agreed shape for each gate: AND, OR, NOT, NAND, NOR, XOR, and XNOR
Bubble	The small circle on a gate's output that inverts it—turning AND into NAND, OR into NOR, and XOR into XNOR
Boolean-algebra law	A rule that rewrites an expression as an equivalent one, such as identity, complement, or absorption
De Morgan's theorem	$\text{NOT}(A \cdot B) = \bar{A} + \bar{B}$ and $\text{NOT}(A + B) = \bar{A} \cdot \bar{B}$; a NOT over a bracket flips AND and OR and inverts each variable
Half adder	Two gates on the same two inputs—an XOR for the sum and an AND for the carry—which add two single bits

Pedagogical Focus

- **Self-Management Skills (ATL):** Students consciously practise self-management by organising a multi-step simplification—one named law per line, working from the inside of the brackets outwards—and by checking their own work by re-tabulating against the original.
- **Assessment (ATT):** This lesson runs on visible evidence. Share at the outset what a correct diagram and a fully simplified expression look like, then use mini-whiteboards and a hinge question partway through to see who has the gate symbols and who is confusing them.

Name the skill to students: *"Today you are managing and checking your own working—the truth table tells you whether you're right without waiting for me."*

EAL Scaffold

Support Type	Description
Gate Symbol Reference Strip	Including XNOR, kept on the desk

Support Type	Description
Fully Worked Simplification	Each law named, kept as a model to imitate
Sentence Frame	"By the [law name] law, [expression] simplifies to [result] because ____."

2. Lesson Sequence (One-Hour Block)

Part 1: Do Now (Retrieval) — ~10%

Activity: Three short recall items:

Question	Source
1. How do you confirm that two circuits are equivalent?	[A1.2.4]
2. Which gate is 1 only when its inputs differ, and which only when they match?	[A1.2.3]
3. NAND, NOR, and XNOR are which three gates with their output inverted?	[A1.2.3]

Part 2: Main Sequence — ~60%

Phase 1: Success Criteria (~5 mins)

What a Correct Diagram Needs:

Criteria	Description
Correct symbol	The agreed shape for each gate
Correct connections	Wires that fix the signal path
Labels	Every input and the output labelled

What "Fully Simplified" Means:

- Each step is a **named law**
- Nothing reduces further
- The result can be **verified** by re-tabulation (truth table)

Phase 2: The Seven Symbols and a Hinge Check (~10 mins)

The Three Building Blocks:

Gate	Symbol	Rule
AND		1 only when both inputs are 1
OR		1 when either input is 1 (including both)
NOT		Flips its single input

The Bubble Rule — Derived Gates:

Gate	Relationship	Rule
NAND	AND + bubble	Inverted AND
NOR	OR + bubble	Inverted OR
XNOR	XOR + bubble	Inverted XOR

The Exclusive Pair:

Gate	Rule
XOR	1 only when inputs differ
XNOR	1 only when inputs match

Hinge Question (Whiteboards):

1. "Draw the XNOR symbol."
2. "Which single change turns an OR into a NOR?"
3. "Which gate is 1 only when the inputs match?"

Read the boards and reteach the confusable pairs before moving on.


Phase 3: Construct from an Expression (~15 mins)

Worked Example — Constructing a Diagram:

Construct the diagram for:
 $Z = (A \cdot B) + \bar{C}$

Step-by-Step Construction:

Step	Action
1	Work from inside the brackets outwards
2	Draw the AND gate for $A \cdot B$
3	Draw the NOT gate for $\bar{C}$
4	Draw the OR gate to combine them
5	Label every input and the output

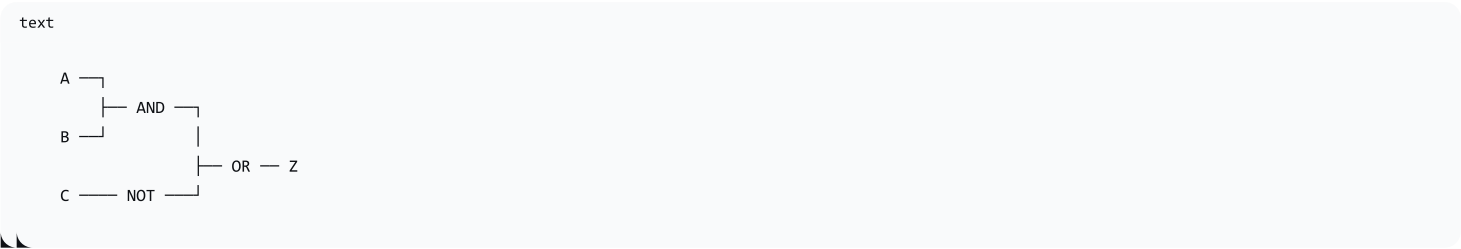


Student Task: Construct a diagram from a given expression and **self-check** against the criteria.

The Half Adder — Combining Gates:

Operation	Gate	Expression
Sum	XOR	Sum = $A \oplus B$
Carry	AND	Carry = $A \cdot B$

Half Adder Diagram:

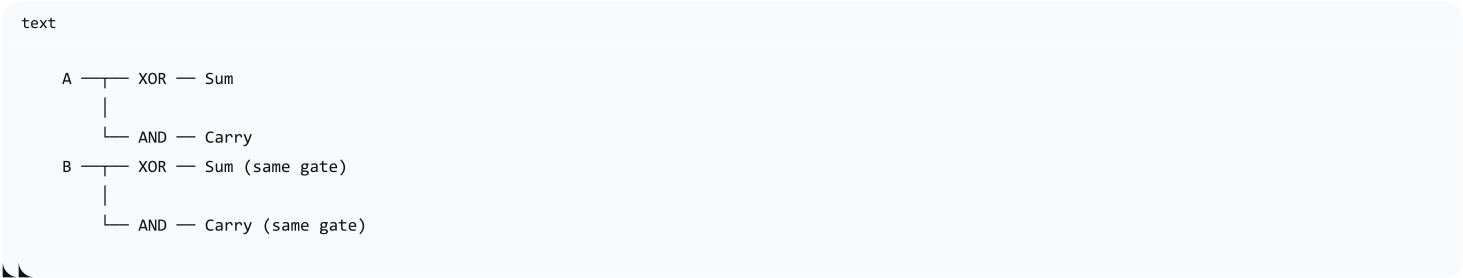

"Two single bits are added: the XOR gives the sum, and the AND gives the carry."

Phase 4: Simplify by Boolean Law (~15 mins)

The Laws of Boolean Algebra:

Law	Form 1 (AND)	Form 2 (OR)
Annulment	$A \cdot 0 = 0$	$A + 1 = 1$
Identity	$A \cdot 1 = A$	$A + 0 = A$
Complement	$A \cdot \bar{A} = 0$	$A + \bar{A} = 1$
Idempotent	$A \cdot A = A$	$A + A = A$
Double Negation	$\bar{\bar{A}} = A$	
Absorption	$A \cdot (A + B) = A$	$A + (A \cdot B) = A$
Distributive	$A \cdot (B + C) = A \cdot B + A \cdot C$	$A + (B \cdot C) = (A+B) \cdot (A+C)$
De Morgan	$A \cdot B = \bar{\bar{A} + \bar{B}}$	$A + B = \bar{\bar{A} \cdot \bar{B}}$

Worked Simplification — Named Laws:

Step	Expression	Law Used
1	$Z = (A \cdot \bar{B}) + (A \cdot B)$	Original
2	$Z = A \cdot (\bar{B} + B)$	Distributive (factor A)
3	$Z = A \cdot 1$	Complement
4	$Z = A$	Identity

Connecting Back to A1.2.4:

"From the previous lesson, $(A + B) \cdot (A + C)$ simplifies to $A + B \cdot C$ by the distributive law—the same result the Karnaugh map gave."

Student Task: Simplify one expression, naming each law, and **verify by re-tabulating** against the original.

Part 3: Deliberate Practice — ~20%

Activity (Pairs):

Task	Description
Task 1	Construct a diagram from a given expression; mark against the three criteria
Task 2	Simplify a given expression; name each law and confirm the result by truth table

Sentence Frame for Naming Laws:

By the [law name] law, [expression] simplifies to [result] because ____.

Part 4: Exit Check — ~10%

Two Items (Readable in Minutes):

Question	Purpose
Part A: "Construct the diagram for $Z = A \cdot (B + C)$ "	Checks diagram construction against three criteria
Part B: "Simplify $Z = A \cdot B + A \cdot \bar{B}$, naming each law"	Checks simplification with named laws

Expected Answer (Part B):

Step	Expression	Law Used
1	$Z = A \cdot B + A \cdot \bar{B}$	Original
2	$Z = A \cdot (B + \bar{B})$	Distributive
3	$Z = A \cdot 1$	Complement
4	$Z = A$	Identity

Mark Part A against the three diagram criteria (symbol, connections, labels).

3. Complete Reference: Seven Gate Symbols

Gate	Symbol Shape	Rule	Inversion
AND	D-shape	1 only when both inputs are 1	No
OR	Curved D-shape	1 when either input is 1 (including both)	No
NOT	Triangle with bubble	Flips its single input	Bubble on output
NAND	AND with bubble	Inverted AND	Bubble on output
NOR	OR with bubble	Inverted OR	Bubble on output
XOR	OR with extra curve	1 only when inputs differ	No

Gate	Symbol Shape	Rule	Inversion
XNOR	XOR with bubble	1 only when inputs match	Bubble on output

Common Confusions to Address:

Confusion	Distinction
OR vs. XOR	OR = 1 if either (including both); XOR = 1 only if exactly one
XOR vs. XNOR	XNOR is XOR inverted; XNOR = 1 when inputs match
AND vs. NAND	NAND is AND inverted; NAND = 0 only when both inputs are 1

4. Boolean Algebra Laws Summary

Law	AND Form	OR Form
Annulment	$A \cdot 0 = 0$	$A + 1 = 1$
Identity	$A \cdot 1 = A$	$A + 0 = A$
Complement	$A \cdot \bar{A} = 0$	$A + \bar{A} = 1$
Idempotent	$A \cdot A = A$	$A + A = A$
Double Negation	$\bar{\bar{A}} = A$	
Absorption	$A \cdot (A + B) = A$	$A + (A \cdot B) = A$
Distributive	$A \cdot (B + C) = A \cdot B + A \cdot C$	$A + (B \cdot C) = (A+B) \cdot (A+C)$
De Morgan	$\overline{A \cdot B} = \bar{A} + \bar{B}$	$\overline{A + B} = \bar{A} \cdot \bar{B}$

Order of Operations for Boolean Algebra:

1. Brackets (parentheses) — innermost first
2. NOT ($\bar{}$)
3. AND ($\cdot$)
4. OR ($+$)

5. Differentiation & Extension

Support (Removable Scaffolding)

Support Strategy	Description
Gate Symbol Reference Strip	Including XNOR; kept on the desk
Fully Worked Simplification	Each law named; kept as a model to imitate
Sentence Frame	For naming a law; withdrawn once students name them unprompted

Challenge (Deeper and Wider, Not Merely More)

Challenge Strategy	Description
Apply De Morgan	Apply De Morgan's theorem to a bracket before simplifying
Count Gates Saved	Construct a diagram, simplify it, construct the reduced diagram, and count the gates saved
Link to Truth Tables	Confirm that the original and reduced diagrams are equivalent by truth table (links algebra route back to A1.2.4)

6. Example Hinge Questions

Question	Purpose
"What are the three core logical operations you know?"	Activates prior knowledge
"Draw the XNOR symbol."	Checks recognition of full set of seven gates
"Which single change turns an OR into a NOR?"	Checks understanding of the bubble rule
"Which gate is 1 only when the inputs match?"	Checks understanding of XNOR
"Which law would you use first to simplify $A \cdot B + A \cdot \bar{B}$?"	Checks recognition of factoring opportunity
"What is the benefit of simplifying a Boolean expression?"	Checks understanding of purpose (fewer gates)

7. Teacher Notes: Addressing Student Challenges

Potential Challenge	Advice/Strategy
Distinguishing OR and XOR	Emphasise exact phrasing: OR = true if A or B or both; XOR = true if A or B but NOT both. Analogy: "You can have soda OR water (or both)" vs. "You can choose a red shirt XOR a blue shirt (but not both)."
Order of Operations	Write hierarchy on the board: 1. Brackets, 2. NOT, 3. AND, 4. OR. Students must follow this strictly.
Applying Boolean Laws	Advise students to look for patterns: Complements ($A + \bar{A} \rightarrow 1$), Common terms to factor (Distributive), Redundancy (Absorption).
Connecting Algebra to Diagrams	Continually remind students that every term removed is a physical gate saved. Show "before" (complex) and "after" (simplified) diagram side by side.

8. Learning Objectives (Summary)

Knowledge and Understanding

- Identify and state the function of the standard logic gate symbols (AND, OR, NOT, NAND, NOR, XOR, XNOR)
- Apply the laws of Boolean algebra to simplify logical expressions
- Understand how combinations of gates perform complex operations (half adder)

ATL Skills

Skill	Description
Self-Management	Organise multi-step simplification; check own work by re-tabulation
Thinking	Apply critical thinking to simplify complex expressions
Communication	Present simplification clearly with named laws

9. Resources

- Presentation (Slide Deck)
- InThinking eBook (A1.2.5)
- Worksheet: Diagram construction + Boolean simplification
- Worksheet Answers

Author's Reflection

"The main change is that XNOR is now included. The material I started from listed six gates and left it out, so the full set of seven that the syllabus names is taught together. I also gave more of the lesson to students actually drawing circuits, since the command term is Construct and the earlier deck spent most of its time on the gate symbols and the laws rather than on building a diagram.

The laws table and the worked simplifications were already sound, so I kept them and added a set of practice questions, because the laws only stick with use. I added one simple check as well: once students simplify an expression, they build the truth table for their answer and compare it with the original, which tells them whether they are right. The lesson ends by returning to the two circuits from the previous lesson and simplifying one to $A + B \cdot C$ by algebra, so the truth table, the Karnaugh map, and the laws all reach the same place."